

supplementary material on the Tiny Register Machine Implementation

not be covered in class

4.3 BEHIND THE SCENES OF ACTIVE CELLS

TRM Architectural State

- PC
- 8 registers
- flag registers
- Memory (configurable)
 - $nK * 36$ bits instruction memory ($1k = 1024$)
 - $nk * 32$ bits data memory

PL vs. HDL

Programming Language

- Sequential execution
- No notion of time

```
var a,b,c: integer;  
a := 1;  
b := 2;  
c := a + b;
```

} unknown
mapping
to machine
cycles

Hardware Description Language

- Continuous execution (combinational logic)

```
wire [31:0] a,b,c;
```

```
assign a=1;  
assign b=2;  
assign c=a+b;
```

} no memory
associated

- Synchronous execution (register transfer)

```
reg [31:0] a,b,c;
```


```
always @ (posedge clk)  
begin
```

```
    a <= 1;  
    b <= 2;  
    c <= a+b;
```

```
end;
```

} synchronous
at rising edge of
the clock

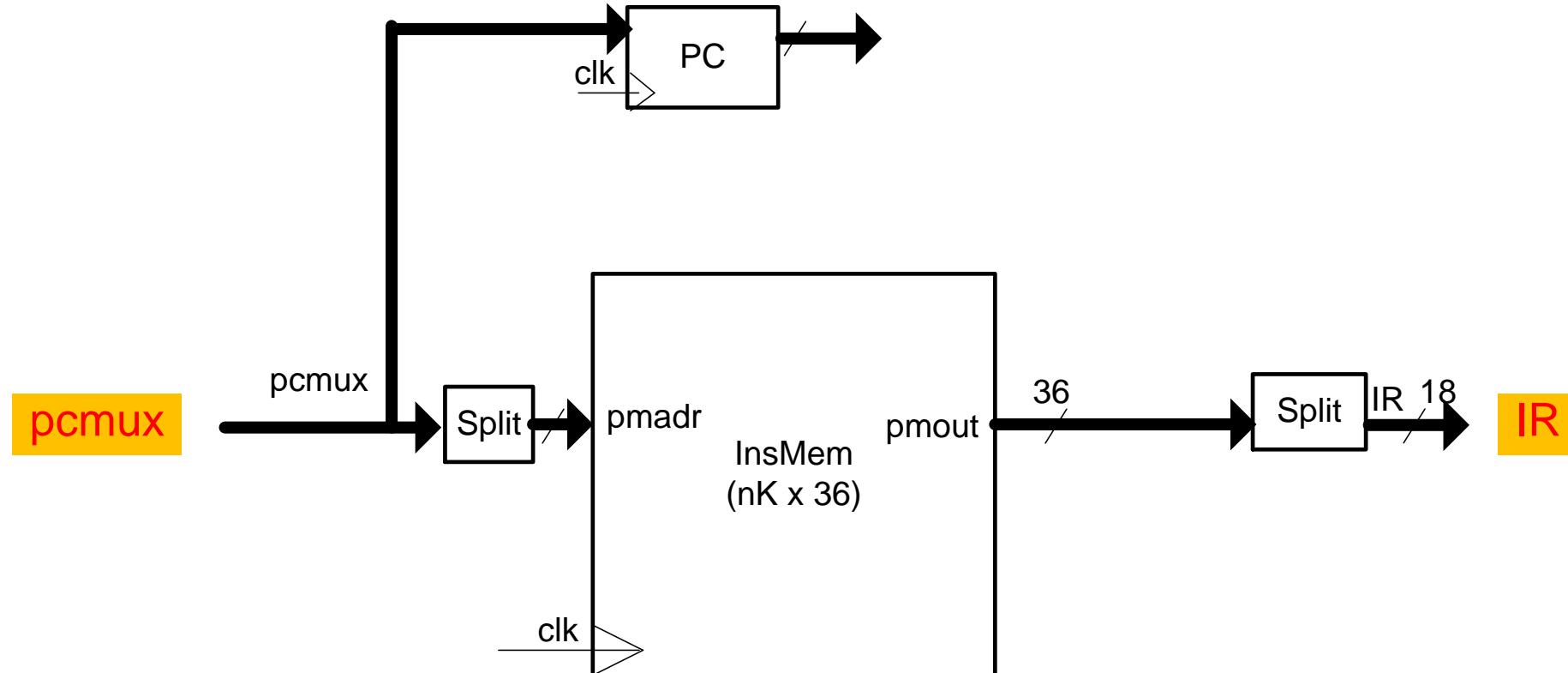Single-Cycle Datapath: arithmetical logical instruction fetch



Single-Cycle Datapath: instruction fetch

```
wire [PAW-1:0] pcmux, nxpc;
wire [17:0] IR;
reg [PAW-1:0] PC;


IM #(.BN(IMB)) imx(.clk(clk), .pmadr({{{32-PAW}{1'b0}}},pcmux[PAW-1:1]),
    .pmout(pmout));

assign IR = (~rst)? NOP: (PC[0]) ? pmout[35:18] : pmout[17:0];

always @ (posedge clk) begin
    if (~rst) PC <= 0;
    else if (stall0)
        PC <= PC;
    else
        PC <= pcmux;
end
```

Single-Cycle Datapath: register read

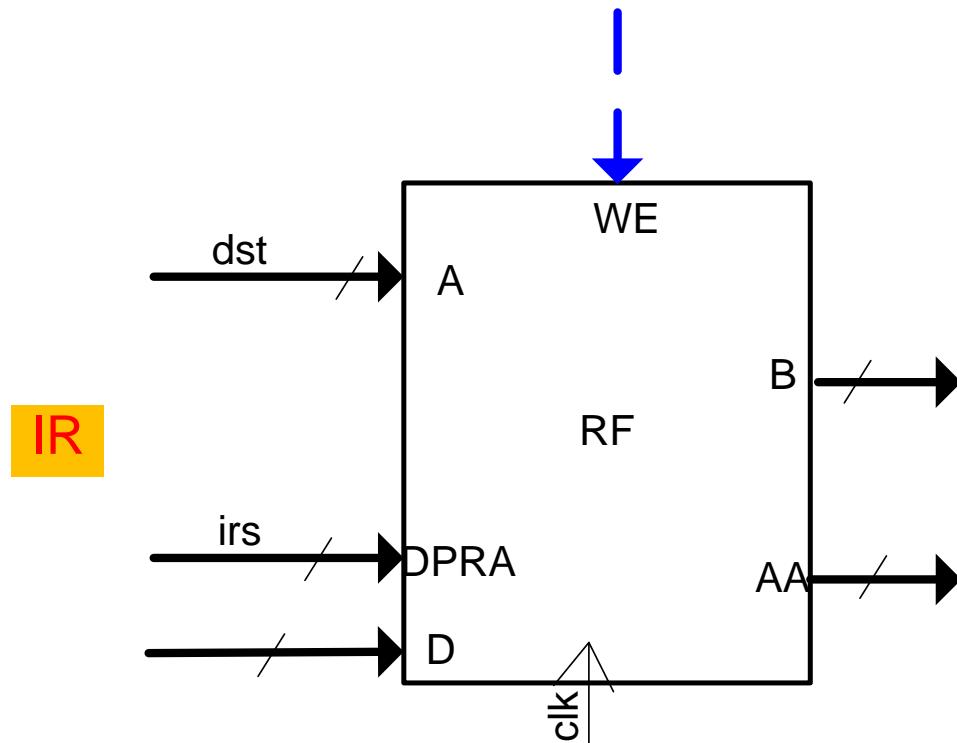- STEP 2: Read source operands from register file



```


wire [2:0] rd, rs;
wire regWr;
wire [31:0] rdOut, rsOut;

//register file
...
assign irs = IR[2:0];
assign ird = IR[13:11];
assign dst = (BL)? 7: ird;

```

Single-Cycle Datapath: ALU

- STEP 3: Compute the result via ALU

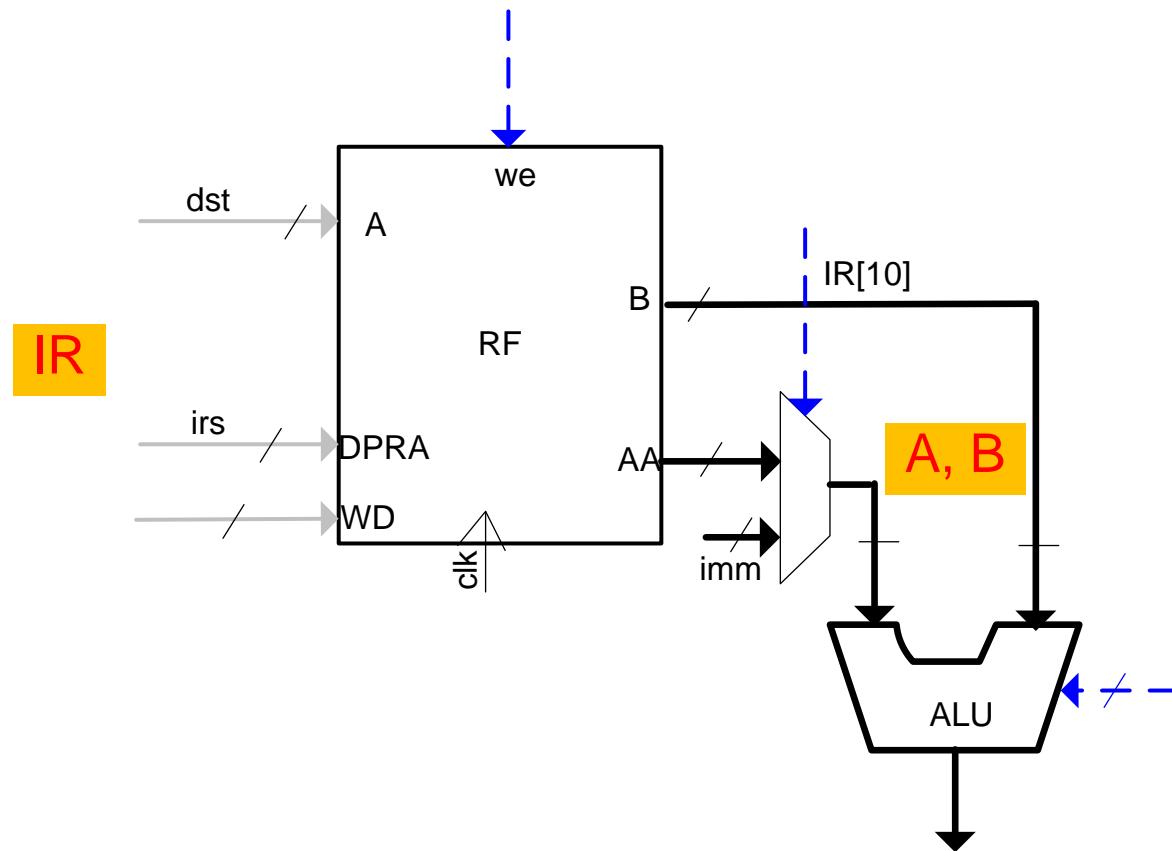

```
wire [31:0] AA, A, B, imm;
wire [32:0] aluRes;

assign A = (IR[10])? AA:
{22'b0, imm};

assign minusA = {1'b0, ~A} + 33'd1;
assign aluRes =
(MOV)? A:
(ADD)? {1'b0, B} + {1'b0, A} :
(SUB)? {1'b0, B} + minusA :
(AND)? B & A :
(BIC)? B & ~A :
(OR)? B | A :
(XOR)? B ^ A :
~A;
```


Control Path

```
assign vector = IR[10] & IR[9] & ~IR[8] & ~IR[7];  
assign op = IR[17:14];  
  
assign MOV = (op == 0);  
assign NOT = (op == 1);  
assign ADD = (op == 2);  
assign SUB = (op == 3);  
assign AND = (op == 4);  
assign BIC = (op == 5);  
assign OR = (op == 6);  
assign XOR = (op == 7);  
assign MUL = (op == 8) & (~IR[10] | ~IR[9]);  
assign ROR = (op == 10);  
assign BR = (op == 11) & IR[10] & ~IR[9];  
assign LDR = (op == 12);  
assign ST = (op == 13);  
assign Bc = (op == 14);  
assign BL = (op == 15);  
assign LDH = MOV & IR[10] & IR[3];  
assign BLR = (op == 11) & IR[10] & IR[9];
```

IR _{17:14}	Function
0000	B := A
0001	B := ~A
0010	B := B + A
0011	B := B - A
0100	B := B & A
0101	B := B & ~A
0110	B := B A
0111	B := B ^ A

Single-Cycle Datapath: write back to Rd

- **STEP 4:** Write result back to Rd

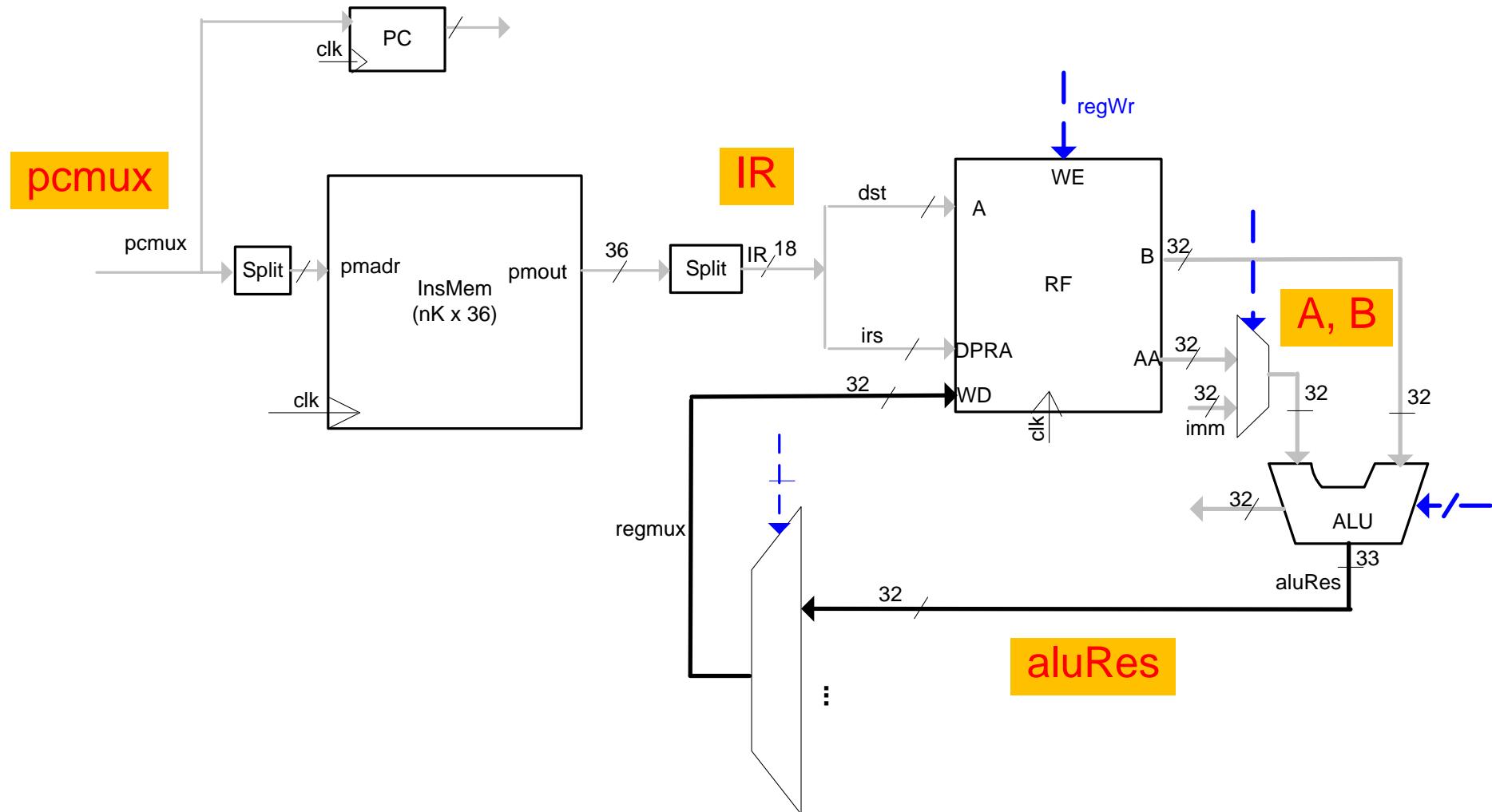


Single-Cycle Datapath: write back to Rd

```
wire [31:0] regmux;  
wire regwr;  
  
...  
  
assign regwr = (BL | BLR | LDR & ~IR[10] |  
    ~(IR[17] & IR[16]) & ~BR & ~vector)) & ~stall0;  
  
assign regmux =  
    (BL | BLR) ? {{32-PAW}{1'b0}}, nxpc :  
    (LDR & ~loenbReg) ? dmout :  
    (LDR & loenbReg)? InbusReg: //from IO  
    (MUL) ? mulRes[31:0] :  
    (ROR) ? s3 :  
    (LDH) ? H :  
    aluRes;
```


Single-Cycle Datapath: LD

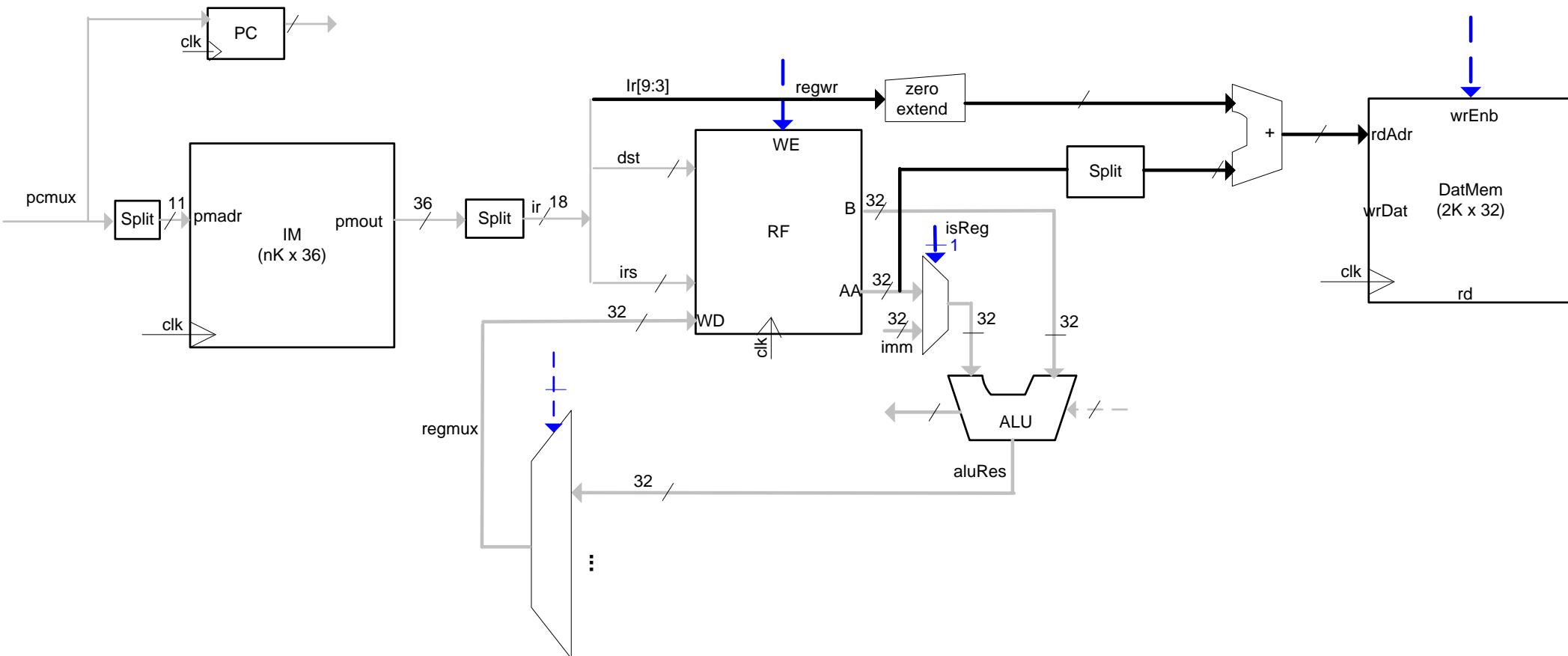- **STEP 1:** Fetch instruction
- **STEP 2:** Read source operand from the register file
- **STEP 3:** Compute the memory address



Single-Cycle Datapath: LD

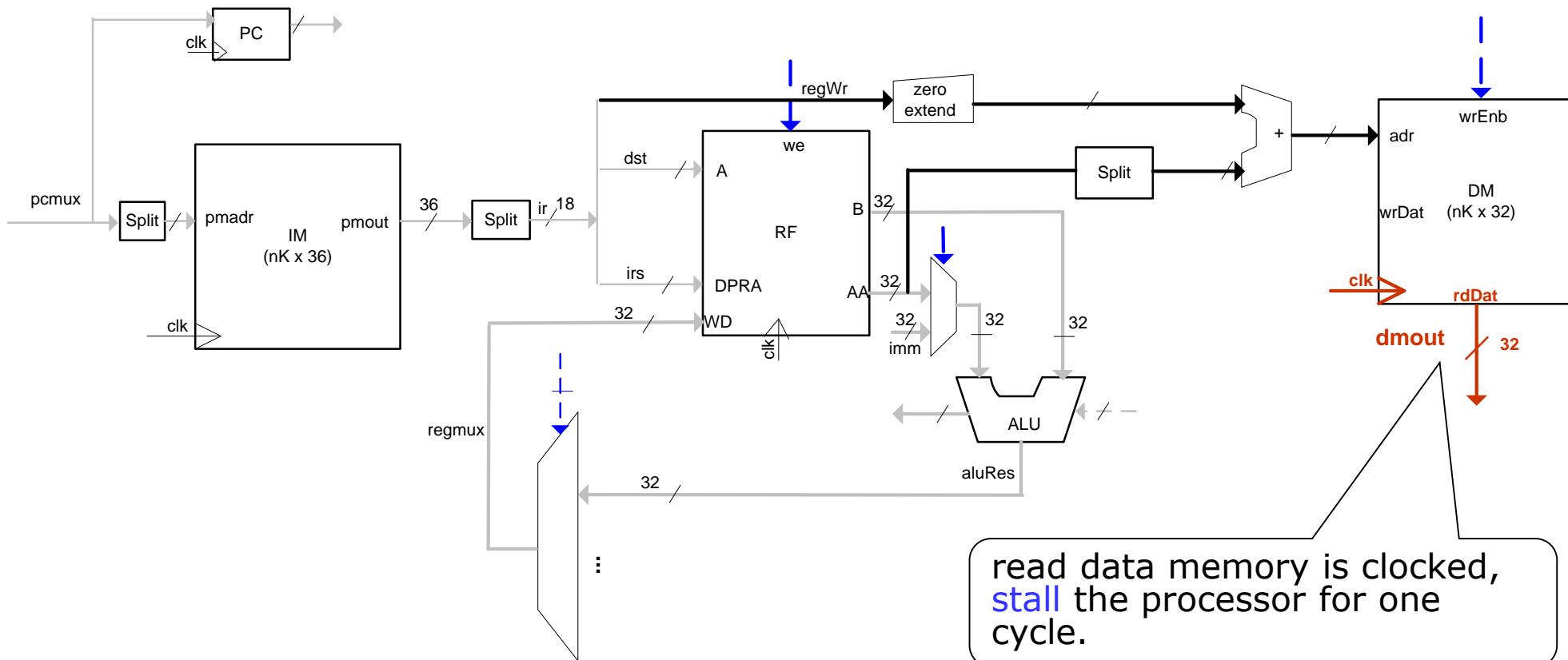- **STEP 3:** Compute the memory address
- **STEP 4:** Read data from data memory




TRM Stalling

- stop fetching next instruction, pcmux keeps the current value
- disable register file write enable and memory write enable signals to avoid changing the state of the processor.
 - only LD and MUL instructions stall the processor.
 - **dmwe** signal is not affected.
 - **regwr** signal is affected.

Single-Cycle Datapath: LD

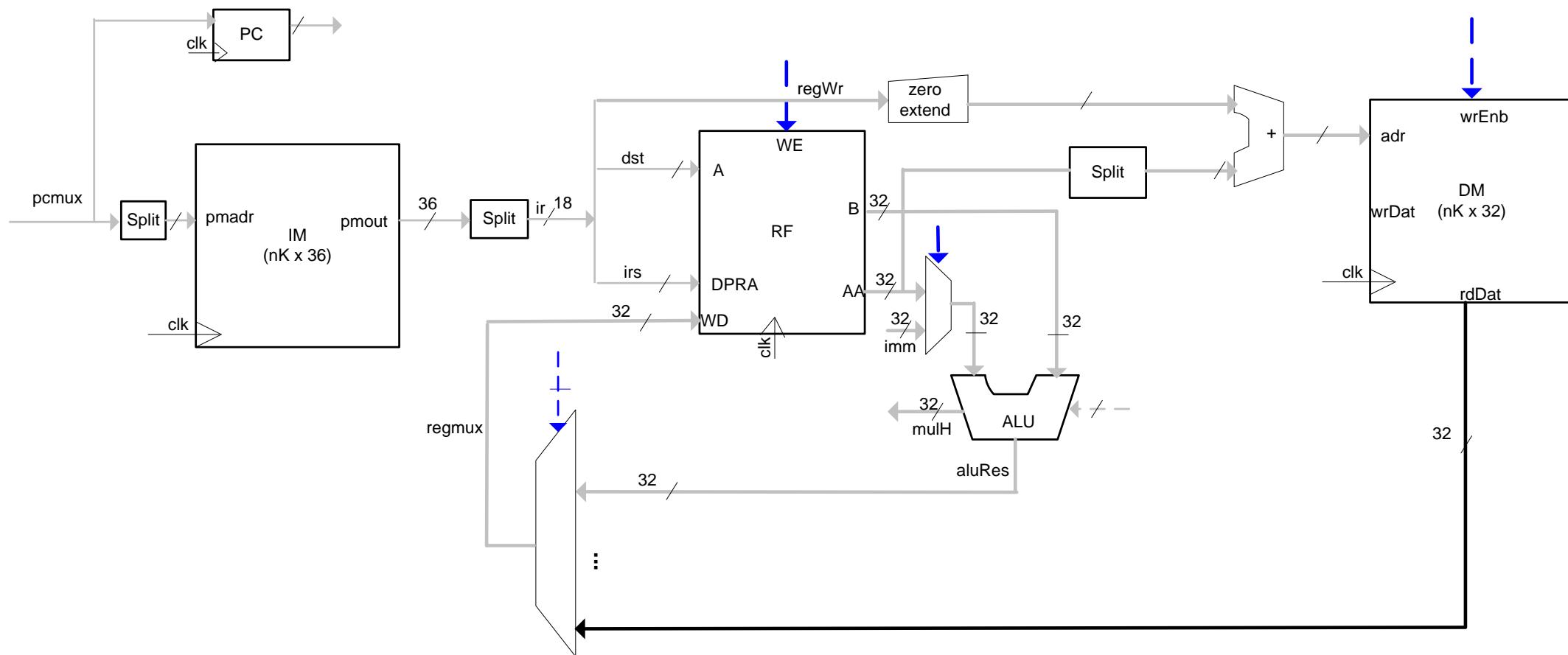- STEP 4: Read data from data memory
- STEP 5: Write data back into the register file



TRM: LD

Verilog code in TRM module

```
wire [31:0] dmout;
wire [DAW:0] dmadr;
wire [6:0] offset;
reg IoenbReg;

//register file
...
Assign dmadr = (irs == 7) ? {{{DAW-6}{1'b0}}, offset} : (AA[DAW:0] + {{{DAW-6}{1'b0}}, offset});
assign ioenb = &(dmadr[DAW:6]);
assign rfWd = ...
    (LDR & ~IoenbReg) ? dmout:
    (LDR & IoenbReg) ? InbusReg: //from IO
    ...;
always @ (posedge clk)
    IoenbReg <= ioenb;
```


LD rd, [rs+offset]

Src register = lr ignored
(Harvard architecture!)

I/O space: Uppermost
2⁶ bytes in data
memory

Single-Cycle Datapath: ST

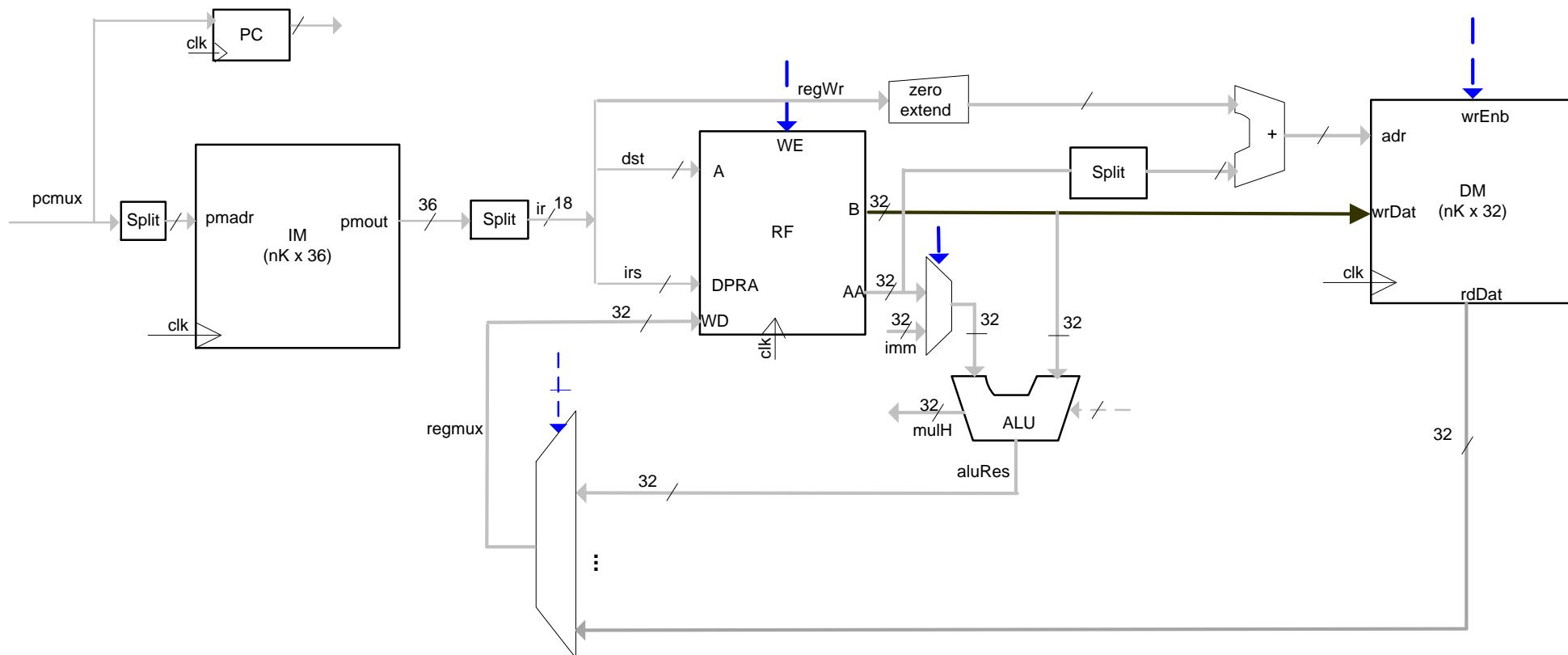- **STEP 1:** Fetch instruction
- **STEP 2:** Read source operand from the register file
- **STEP 3:** Compute the memory address
- **STEP 4:** Write data into the data memory



Single-Cycle Datapath: ST


- **STEP 3:** Compute the memory address
- **STEP 4:** Write data into the data memory

```
wire [31:0] dmin;  
wire dmwr;  
  
//register file  
...  
DM #(.BN(DMB)) dmx (.clk(clk),  
    .wrDat(dmin),  
    .wrAddr({{{31-DAW}{1'b0}}},dmadr),  
    .rdAddr({{{31-DAW}{1'b0}}},dmadr),  
    .wrEnb(dmwe),  
    .rdDat(dmout));  
  
Assign dmwe = ST & ~IR[10] & ~ioenb;  
assign dmin = B;
```

Single-Cycle Datapath: set flag registers

```
always @ (posedge clk, negedge rst) begin // flags
    handling
    if (~rst) begin N <= 0; Z <= 0; C <= 0; V <= 0; end
    else begin
        if (regwr) begin
            N <= aluRes[31];
            Z <= (aluRes[31:0] == 0);
            C <= (ROR & s3[0]) | (~ROR & aluRes[32]);
            V <= ADD & ((~A[31] & ~B[31] & aluRes[31])
                         | (A[31] & B[31] & ~aluRes[31]))
                         | SUB & ((~B[31] & A[31] & aluRes[31])
                         | (B[31] & ~A[31] & ~aluRes[31]));
        end
    end
end
```

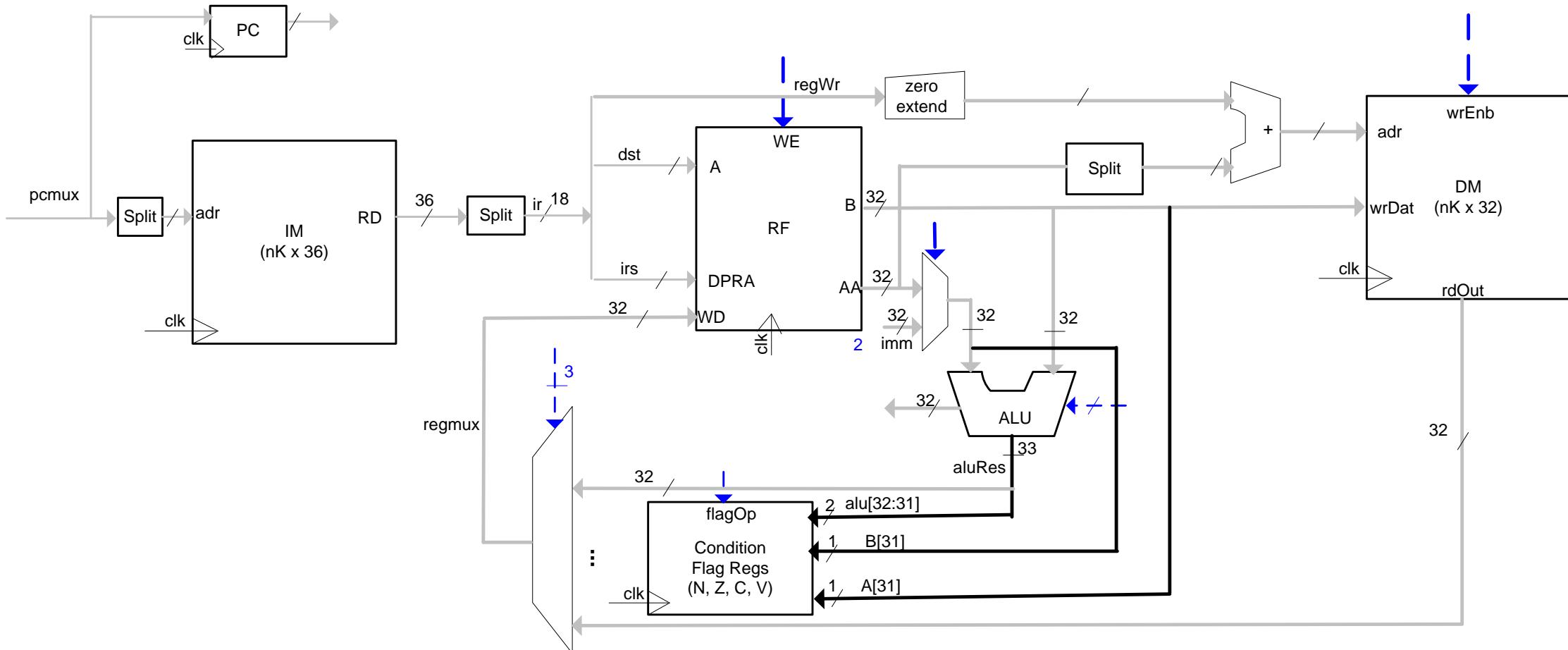
Single-Cycle Datapath: set flag registers



Single-Cycle Datapath: Branch instructions

- Type c instructions, BR instruction, BL instruction
 - $PC \leq PC + 1 + off$
 - $PC \leq Rs$
 - **$PC \leq PC + 1$ (by default)**
 - **$PC \leq PC$ (if stall)**
 - **$PC \leq 0$ (reset)**

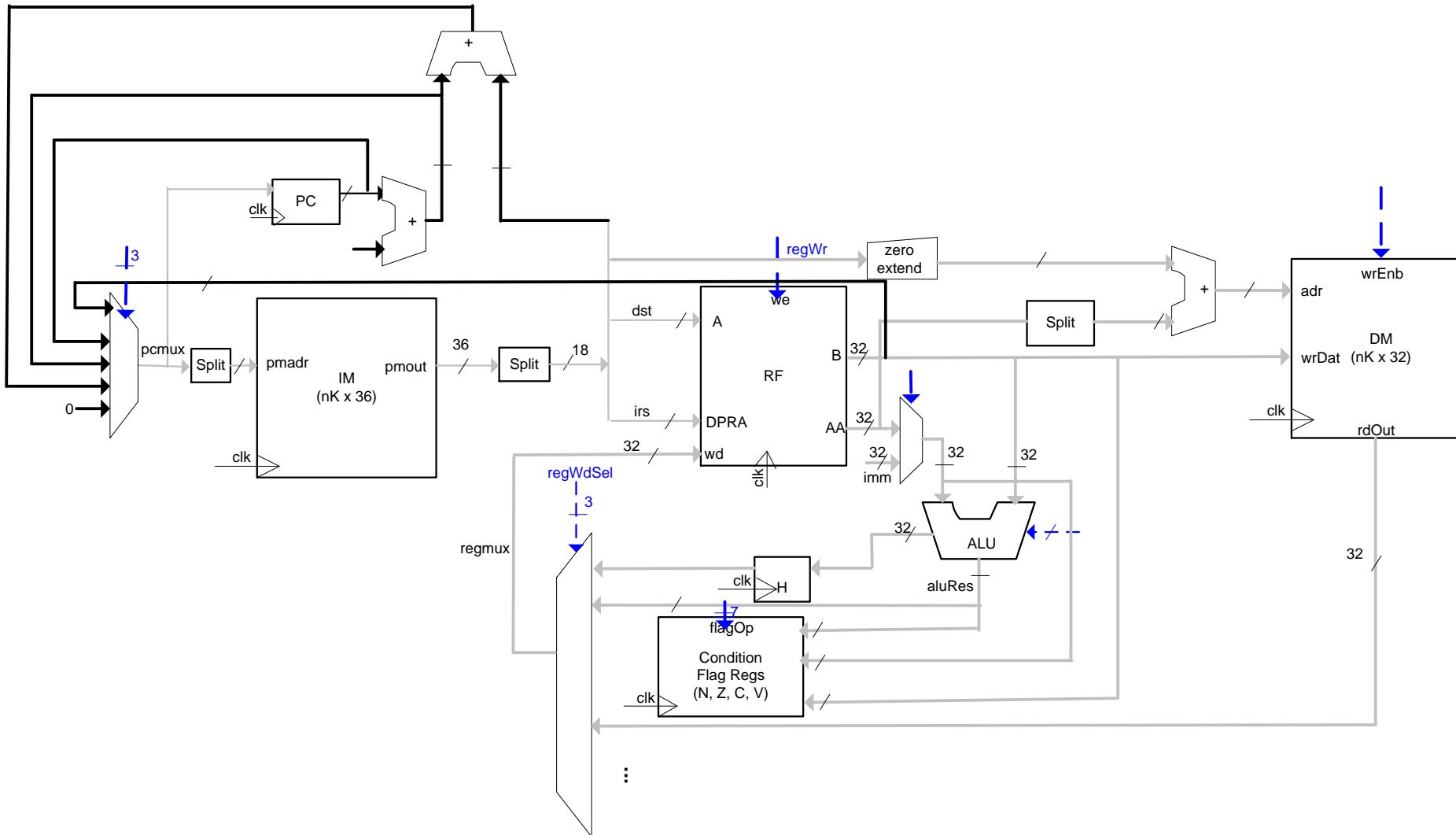Single-Cycle Datapath: Branch instructions



Single-Cycle Datapath: Branch instructions

```
//pcmux logic
assign pcmux =
(~rst) ? 0 :
(stall0) ? PC:
(BL)? {{10{IR[BLS-1]}},IR[BLS-1: 0]}+ nxpc :
(Bc & cond) ? {{PAW-10}{IR[9]}}, IR[9:0]} + nxpc :
(BLR | BR ) ? A[PAW-1:0] :
nxpc;
```

Complete single-cycle datapath

